

## Chapter 6 Series Circuits Notes

In previous units we have learned the four basic parts to make a complete circuit

- The energy source
- The control device
- The conductor
- The load

We have also learned that loads can be connected in

- SERIES
- PARALLEL
- SERIES-PARALLEL COMBINATION

In this unit we will discuss topics like

- Principles of a Series Circuit
  - ***Voltage, Current, Resistance*** and ***Power*** in a series circuit.
- Troubleshooting a series circuit using a voltmeter
  - A ***series*** circuit provides only one path for the electrons to flow
- The electrons flow from the negative side of the energy source through the load to the positive side of the energy source

An ***open*** circuit means the circuit is not complete

- The switch may be in the off position
- A wire could be broke
- The load could be broke
- Could have a loose connection.

Devices like *switches, fuses* and *circuit breakers* are connected in series with the load.

Polarity

- It is necessary to know the ***polarity*** in DC circuits to properly connect some components and instruments (like ***DC meters***) into the circuit.
- In DC circuit the electrons flow from a negative point to a positive point.

### ***VOLTAGE IN A SERIES CIRCUIT***

- The total voltage applied to a series circuit is *automatically spread across the loads* or devices in the circuit.
- The voltage across any load will be that amount needed to force the electrons through the resistance of that load.
- This is called a ***VOLTAGE DROP***

#### Voltage

- Total voltage is equal to the sum of the individual voltage drops....
  
- $E_t = E_1 + E_2 + E_3 \dots$

Ohm's Law states, the *voltage drop* across any load in the circuit is equal to the product of the current through the load and the resistance of that load.

- $E = I \times R$
- E= (Voltage drop across the load)
- I= (Current through the load)
- R= (Resistance of the load)

### ***KIRCHHOFF'S LAW OF VOLTAGE***

- In a series circuit, the sum of the voltage drops across the loads is equal to the total voltage applied to the circuit.

### ***CURRENT IN A SERIES CIRCUIT***

- Kirchhoff's law states that all the ***current*** that flows into a point leaves that point.
  
- Current remains the same through out a series circuit.***

#### Current

- Total current is equal to the current flowing through any of the loads.
  
- It = total current flowing in the circuit.
  
- $I_t = I_1 = I_2 = I_3 \dots$

## **RESISTANCE IN A SERIES CIRCUIT**

- The *total resistance* (of the entire circuit) is the sum of all the resistances in the series circuit.

Total Resistance can be calculated with this formula.

- $R_t = R_1 + R_2 + R_3 \dots$

### Determining an Unknown Voltage

- To find the total voltage use the formula

- $E_t = I_t \times R_t$

- To find the voltage of just one load (R1) use the formula*

- $E_1 = I_1 \times R_1$

*To find the voltage of resistor 2 (R2) use the formula*

$$E_2 = I_2 \times R_2$$

### Determining an Unknown Current

- To find the total current use the formula

- $I_t = E_t / R_t$

- To find the current of just one load (R1) use the formula*

- $I_1 = E_1 / R_1$

*To find the current of resistor 2 (R2) use the formula*

$$I_2 = E_2 / R_2$$

### Determining an Unknown Resistance

- To find the total resistance use the formula

- $R_t = E_t / I_t$

- To find the resistance of just one load (R1) use the formula*

- $R_1 = E_1 / I_1$

*To find the resistance of resistor 2 (R2) use the formula*

$$R_2 = E_2 / I_2$$

### Troubleshooting a Series Circuit

- One of the most common circuit faults in a series circuit is an open. (open-circuit)
- A voltmeter, combined with the knowledge of the laws of voltages, is a quick and easy method of analysis.

### Troubleshooting a Series Circuit with a Voltmeter

- To begin the troubleshooting process, measure to determine if there is voltage at the supply. (If the voltage is good move to the fuse.)
- Take a voltage drop reading across the fuse. *A good fuse will not produce a voltage drop.*
- A blown fuse will produce a voltage drop that is equal to the source voltage.*