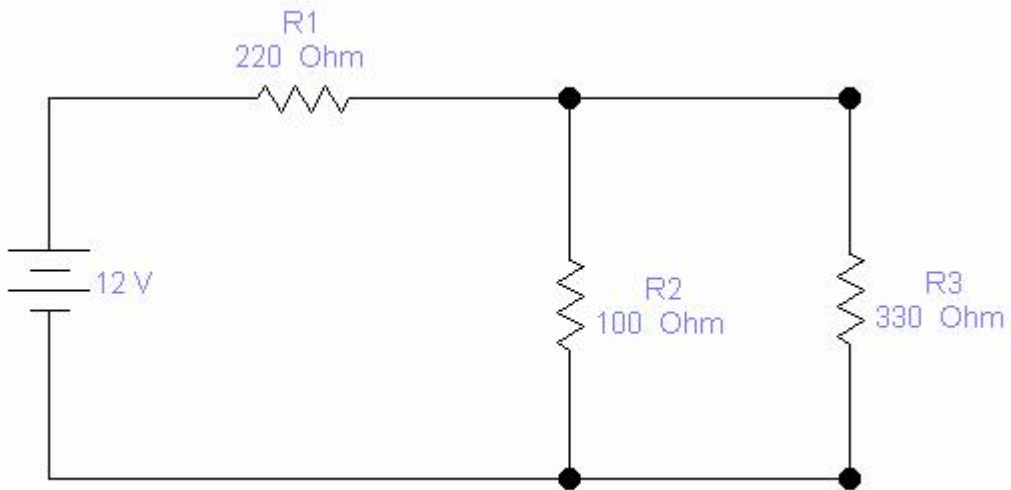


Name: _____

Combination Circuit Ex. 1

Calculate the following:



$R_t =$ _____

$E_t =$ _____

$I_t =$ _____

$R_1 =$ _____

$E_1 =$ _____

$I_1 =$ _____

$R_2 =$ _____

$E_2 =$ _____

$I_2 =$ _____

$R_3 =$ _____

$E_3 =$ _____

$I_3 =$ _____