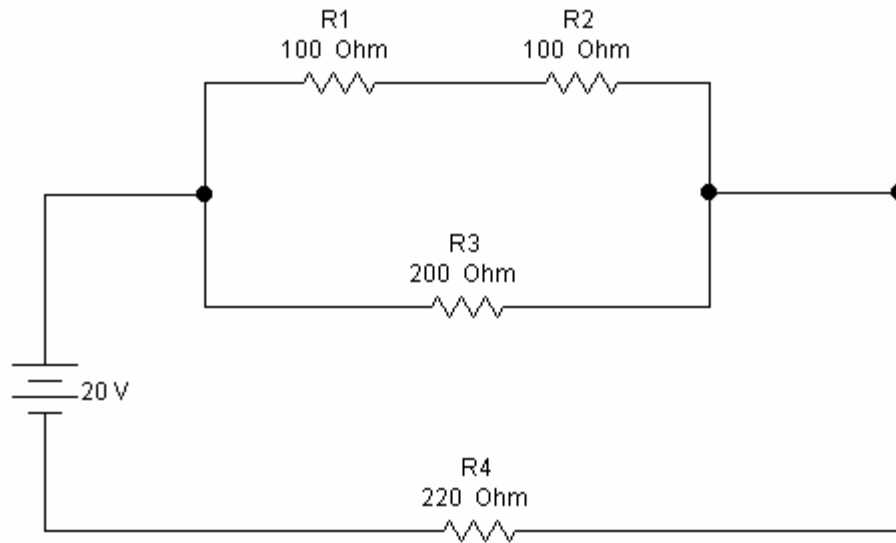


Name: _____

Combination Circuit Ex 5



Calculate the following:

$R_t =$ _____

$E_t =$ _____

$I_t =$ _____

$R_1 =$ _____

$E_1 =$ _____

$I_1 =$ _____

$R_2 =$ _____

$E_2 =$ _____

$I_2 =$ _____

$R_3 =$ _____

$E_3 =$ _____

$I_3 =$ _____

$R_4 =$ _____

$E_4 =$ _____

$I_4 =$ _____

Measure the following:

$R_t =$ _____

$E_t =$ _____

$I_t =$ _____

$R_1 =$ _____

$E_1 =$ _____

$I_1 =$ _____

$R_2 =$ _____

$E_2 =$ _____

$I_2 =$ _____

$R_3 =$ _____

$E_3 =$ _____

$I_3 =$ _____

$R_4 =$ _____

$E_4 =$ _____

$I_4 =$ _____