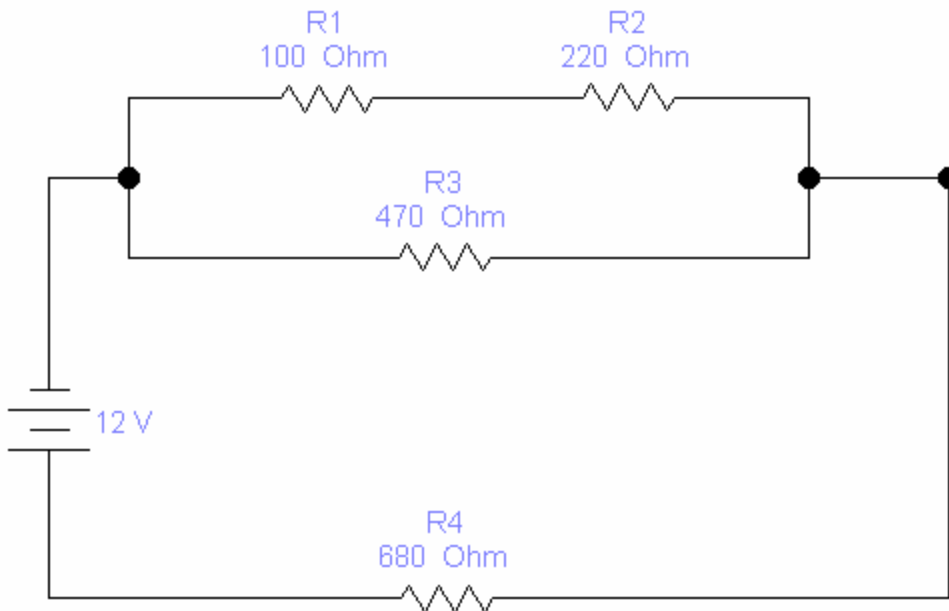


Name: \_\_\_\_\_

### Combination Circuit Ex 9

Calculate the following:



$R_t = \underline{\hspace{2cm}}$

$E_t = \underline{\hspace{2cm}}$

$I_t = \underline{\hspace{2cm}}$

$R_1 = \underline{\hspace{2cm}}$

$E_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$R_2 = \underline{\hspace{2cm}}$

$E_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$R_3 = \underline{\hspace{2cm}}$

$E_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

$R_4 = \underline{\hspace{2cm}}$

$E_4 = \underline{\hspace{2cm}}$

$I_4 = \underline{\hspace{2cm}}$