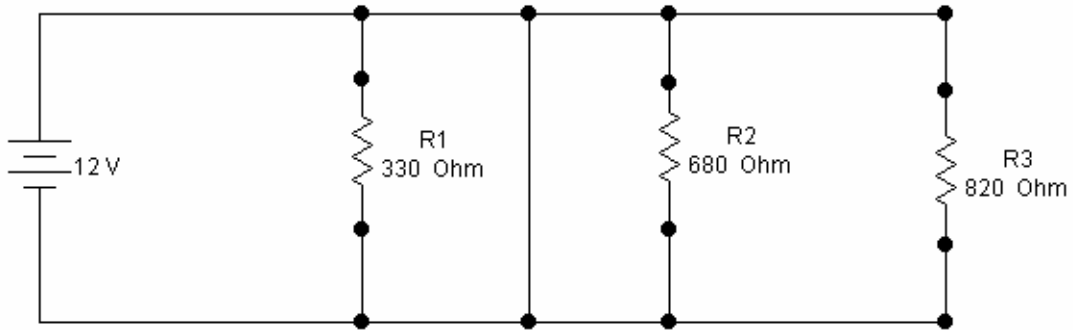


Name: _____

Parallel Circuit Ex 6



Calculate the following:

$R_t = \underline{\hspace{2cm}}$

$E_t = \underline{\hspace{2cm}}$

$I_t = \underline{\hspace{2cm}}$

$R_1 = \underline{\hspace{2cm}}$

$E_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$R_2 = \underline{\hspace{2cm}}$

$E_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$R_3 = \underline{\hspace{2cm}}$

$E_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$

Measure the following:

$R_t = \underline{\hspace{2cm}}$

$E_t = \underline{\hspace{2cm}}$

$I_t = \underline{\hspace{2cm}}$

$R_1 = \underline{\hspace{2cm}}$

$E_1 = \underline{\hspace{2cm}}$

$I_1 = \underline{\hspace{2cm}}$

$R_2 = \underline{\hspace{2cm}}$

$E_2 = \underline{\hspace{2cm}}$

$I_2 = \underline{\hspace{2cm}}$

$R_3 = \underline{\hspace{2cm}}$

$E_3 = \underline{\hspace{2cm}}$

$I_3 = \underline{\hspace{2cm}}$