


Name: _____

Date: _____

Chapter 4

Review Questions for Section 4.1

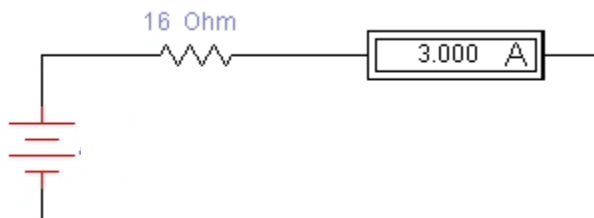1. Define work.
2. Define power.
3. What is the symbol for power? _____
4. What is the unit of electrical power? _____
5. Define horsepower.
6. State Watt's law. Use it in a formula with a given voltage and current.
7. Compute the voltage and the power for the following figure.



E= _____ volts P= _____ watts